

3TB4  
Prelab 3  
March 2, 2018  
Chris Adams - 001403187

**Question 1:**

8 kHz = 8000 Hz = 8000 samples/sec = 8 samples/ms

Student number last two numbers: 87

87ms \* 8 samples/ms  
=696 samples

**Question 3: Mux**

```
module multiplexer(input [15:0] a, input [15:0] b, input [15:0] c, input [1:0] sel, output reg [15:0] r);
```

```
//declare 3 16-bit buses  
wire [15:0] bus_2_d [2:0];
```

```
//bus one connects to 16 bit input a  
assign bus_2_d[0] = a;
```

```
//bus two connects to 16 bit input b  
assign bus_2_d[1] = b;
```

```
//bus three connects to 16 bit input c  
assign bus_2_d[2] = c;
```

```
//always block implements a multiplexer that selects between 3  
always @(*)  
begin  
  case (sel)  
    2'b00: r = bus_2_d[0];  
    2'b01: r = bus_2_d[1];  
    2'b10: r = bus_2_d[2];  
  endcase  
end  
endmodule
```

#### Question 4: fir

```
module fir(input numTaps, input [15:0] d, output reg[15:0] out, clock);
    reg[15:0] coeffs[numTaps-1:0];
    reg[15:0] taps[numTaps-1:0];
    always @(posedge clock)
        begin
            for (i=0;i<numTaps-1;i=i+1)
                begin
                    taps[i+1] <= taps[i];
                end
            taps[0] = d;
            out = 0;
            for (i=0;i<numTaps;i=i+1)
                begin
                    q = q + taps[i]*coeffs[i];
                end
            end
        end
endmodule
```

#### Question 5: echo

```
module echo(input clk, input [15:0] sampleIn, output [15:0] sampleOut);

    wire[15:0] delay, divdelay, feedback;
    assign feedback = sampleOut;
    assign divdelay = {delay[15], delay[15], delay[15:2]};

    always @(posedge clk)
        begin
            sampleOut = divdelay + sampleIn;
        end
    end
Endmodule
```

#### Question 6: subsystem

```
module dsp_subsystem (input sample_clock, input reset, input [1:0] selector, input [15:0] input_sample, output [15:0] output_sample);

    //assign output_sample = input_sample;
    echo(input_sample,output_c,sample_clock);
    fir(input_sample,output_b, 65, sample_clock);
    multiplexer(input_sample,output_b,output_c,sel,output_sample);

endmodule
```